

CHAPTER 3 DIODES


Chapter Outline

- 3.1 The Ideal Diode
- 3.2 Terminal Characteristics of Junction Diodes
- 3.3 Modeling the Diode Forward Characteristics
- 3.4 Operation in the Reverse Breakdown Region – Zener Diodes
- 3.5 Rectifier Circuits
- 3.6 Limiting and Clamping Circuits

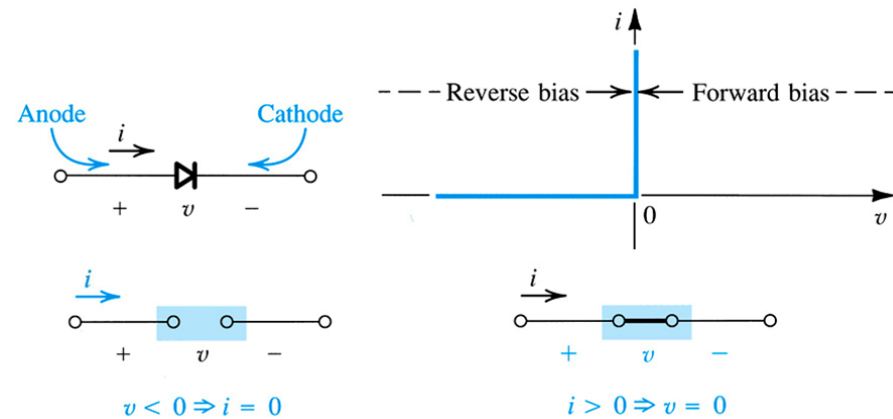
3.1 Ideal Diode

Ideal diode characteristics

- An diode is a two-terminal device:
 - **Anode**: the positive terminal
 - **Cathode**: the negative terminal
- Forward biased \rightarrow turned on \rightarrow short
- Reverse biased \rightarrow turned off \rightarrow open



Circuit applications

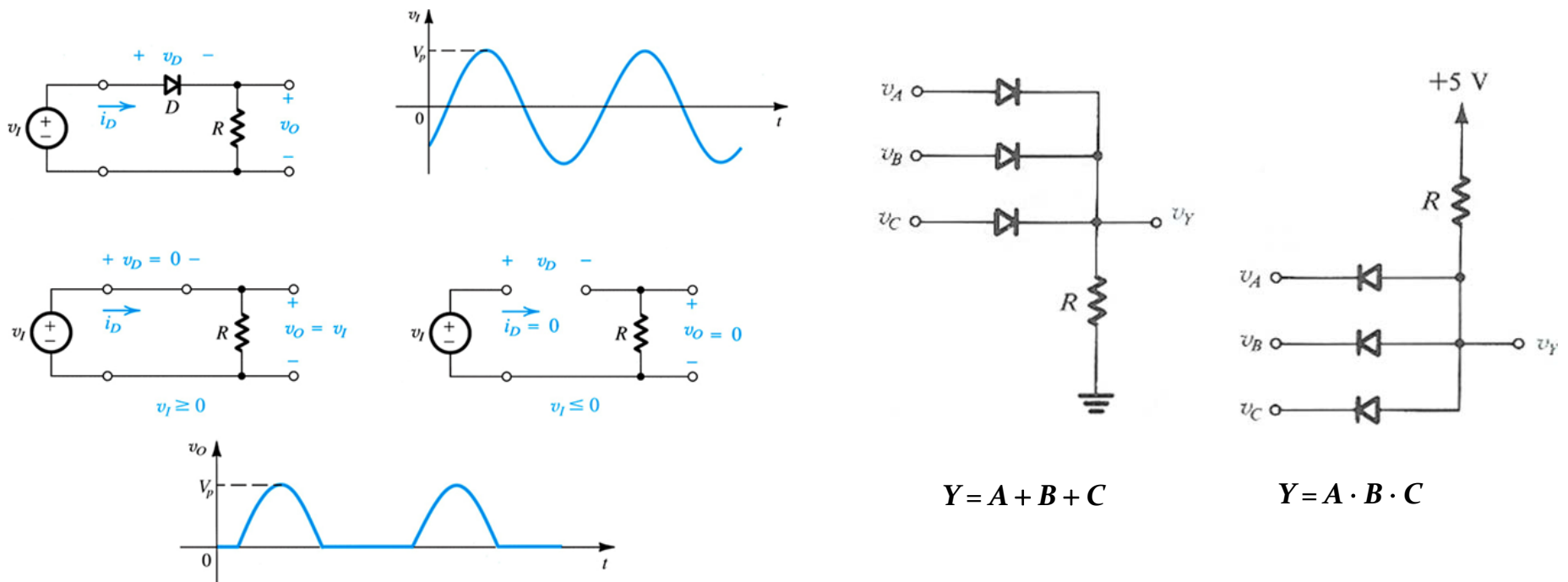

3.2 Terminal Characteristics of Junction Diodes

I-V characteristics of junction diodes


- Diode current: $i = I_S(e^{v/nV_T} - 1)$
 - I_S (saturation current): proportional to diode area
 - n (ideality factor): between 1 and 2
 - V_T (thermal voltage) ≈ 25 mV at room temperature
- The forward-bias region, determined by $v > 0$
- The reverse-bias region, determined by $v < 0$
- The breakdown region, determined by $v < -V_{ZK}$

Forward-bias region

- The simplified forward-bias I-V relationship:
 - For a given forward voltage: $i \approx I_S e^{v/nV_T}$
 - For a given forward current: $v \approx nV_T \ln(I/I_S)$
- Due to the exponential I-V relationship
 - $i \approx 0$ for $v < 0.5$ V (**cut-in voltage**)
 - Fully conduction for 0.6 V $< v < 0.8$ V $\rightarrow V_{on} = 0.7$ V

Temperature dependence

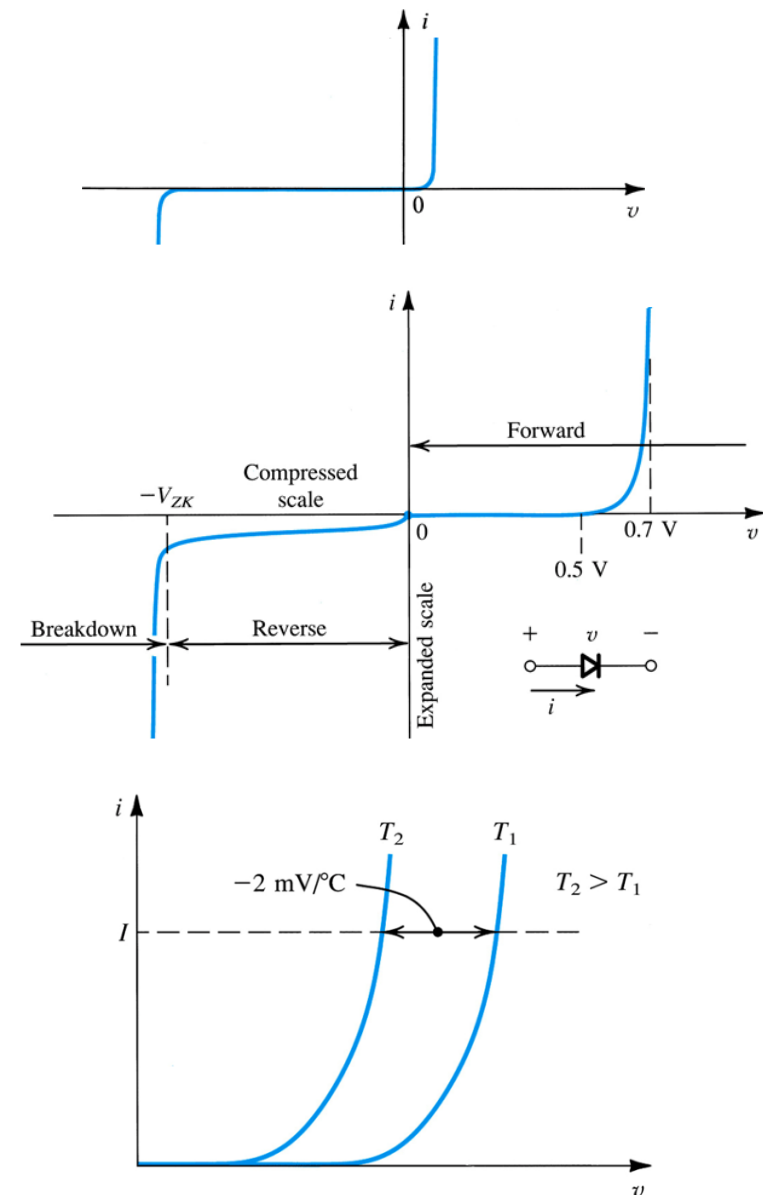- I_S doubles for every 5°C rise in temperature
- Voltage decreases $2\text{mV}/^\circ\text{C}$ for a given current
- Current increases with temperature for a given voltage



Reverse-bias region

- ❑ Reverse current: $i \approx -I_s$
- ❑ Ideally, the reverse current is independent of reverse bias
- ❑ In reality, reverse current is larger than I_s and also increases somewhat with the reverse bias
- ❑ Temperature dependence: reverse current doubles for every 10°C rise in temperature

Breakdown region

- ❑ The knee of the I-V curve is specified as breakdown voltage V_{ZK} for Zener breakdown mechanism
- ❑ In breakdown region, the reverse current increases rapidly with a small increase in the reverse bias
- ❑ Normally, the reverse current is specified by external circuitry to assure the power dissipation within a safe range (non-destructive operation)

3.3 Modeling the Diode Forward Characteristics

Circuit analysis




- ❑ Determine the diode current I_D and voltage V_D for circuit analysis
- ❑ The equation required for the analysis:
 - ➔ $I_D = I_S \exp(V_D/nV_T) \rightarrow$ diode I-V characteristics
 - ➔ $I_D = (V_{DD} - V_D)/R \rightarrow$ Kirchhoff loop equation
- ❑ Need to solve non-linear equations

Graphical analysis

- ❑ Plot the two equations in the same I-V coordination
- ❑ The straight line is known as **load line**
- ❑ The intersect is the solution for I_D and V_D


Iterative analysis

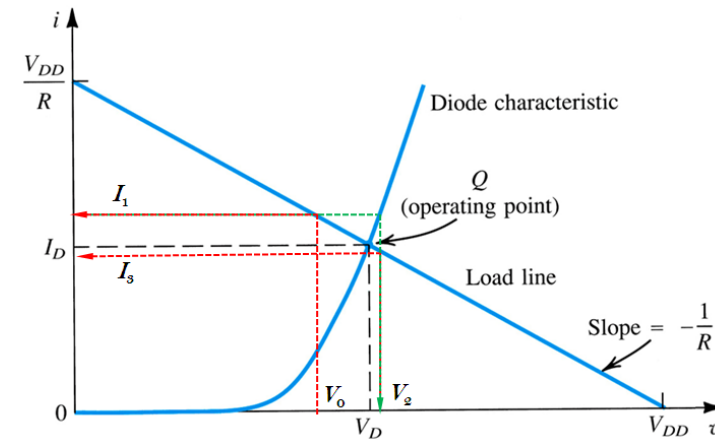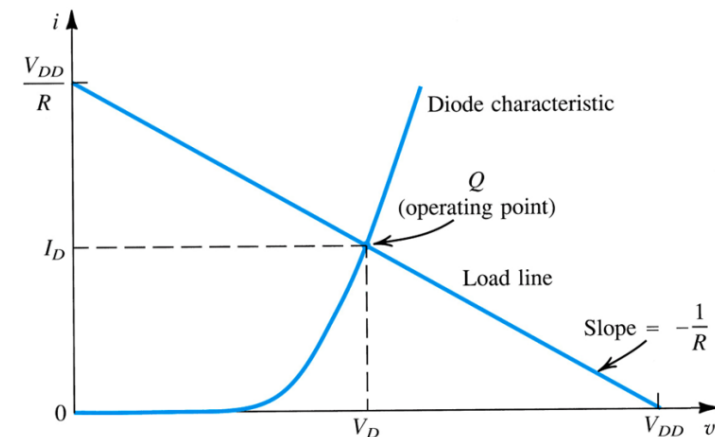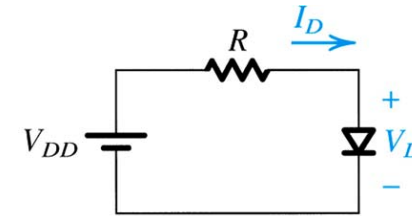- ❑ Set initial value $V_D = V_o$
- ❑ Use $I_D = (V_{DD} - V_D)/R$ to obtain I_1
- ❑ Use $V_D = nV_T \ln(I_D/I_S)$ to obtain V_2
- ❑ Repeat until it converges ($I_3, V_4, I_5, V_6 \dots$)
- ❑ Iterations are needed to solve the nonlinear circuit



The need for rapid analysis

- ❑ Rapid analysis using simplified models for initial design
- ❑ Accurate analysis (iterative analysis or computer program) for final design
- ❑ Rapid analysis (I): ideal-diode model
 - The most simplified model used when supply voltage is much higher than the diode voltage
 - Diode on: $v_D = 0 \text{ V}$ and $i > 0$
 - Diode off: $i = 0$ and $v_D < 0 \text{ V}$
 - Equivalent circuit model as an ideal diode
- ❑ Rapid analysis (II): constant-voltage-drop model
 - The most widely used model in initial design and analysis phases
 - Diode on: $v_D = 0.7 \text{ V}$ and $i > 0$
 - Diode off: $i = 0$ and $v_D < 0.7 \text{ V}$
 - Equivalent circuit model as an ideal diode with a 0.7-V voltage source

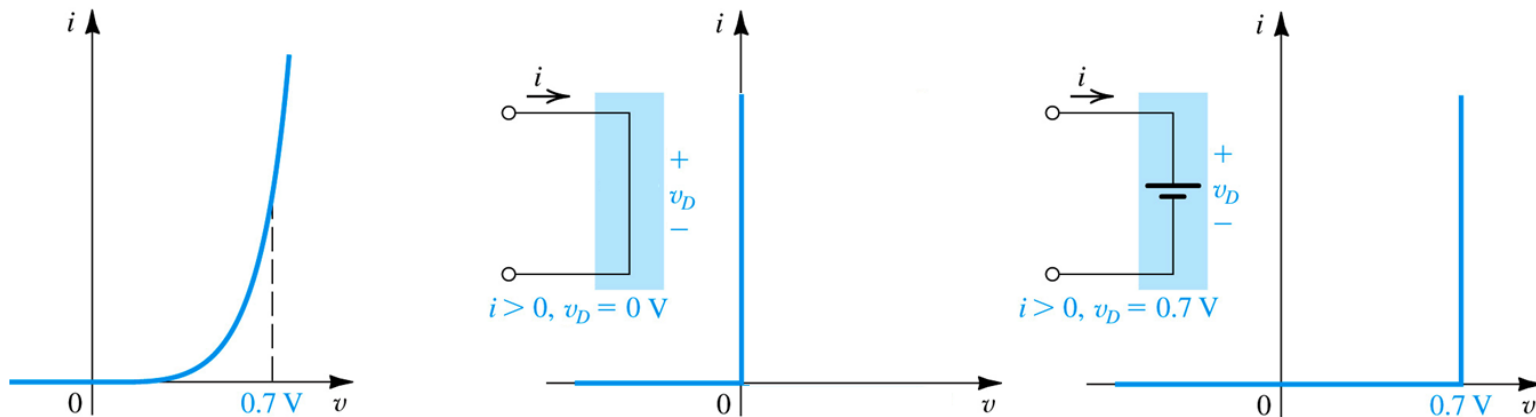

Small-signal approximation

- The diode is operated at a dc bias point and a small ac signal is superimposed on the dc quantities:

$$v_D(t) = V_D + v_d(t)$$

$$i_D(t) = I_S e^{v_D(t)/nV_T} = I_S e^{(V_D + v_d)/nV_T} = I_S e^{V_D/nV_T} e^{v_d/nV_T} = I_D e^{v_d/nV_T}$$

- Under small-signal condition: $v_d / nV_T \ll 1$

$$i_D(t) \approx I_D \left(1 + \frac{v_d}{nV_T}\right) = I_D + \frac{I_D}{nV_T} v_d = I_D + i_d$$

■ I_D associates with $V_D \rightarrow$ dc operating point Q


■ i_d associates with $v_d \rightarrow$ small signal response

- The diode exhibits linear I-V characteristics under small-signal conditions ($v_d \leq 10\text{mV}$)

- Diode **small-signal resistance** and **conductance** at operating point

$$i_d = \frac{I_D}{nV_T} v_d = g_d v_d = v_d / r_d \quad \rightarrow \quad g_d = \frac{I_D}{nV_T} = \left[\frac{\partial i_D}{\partial v_D} \right]_{i_D=I_D}$$
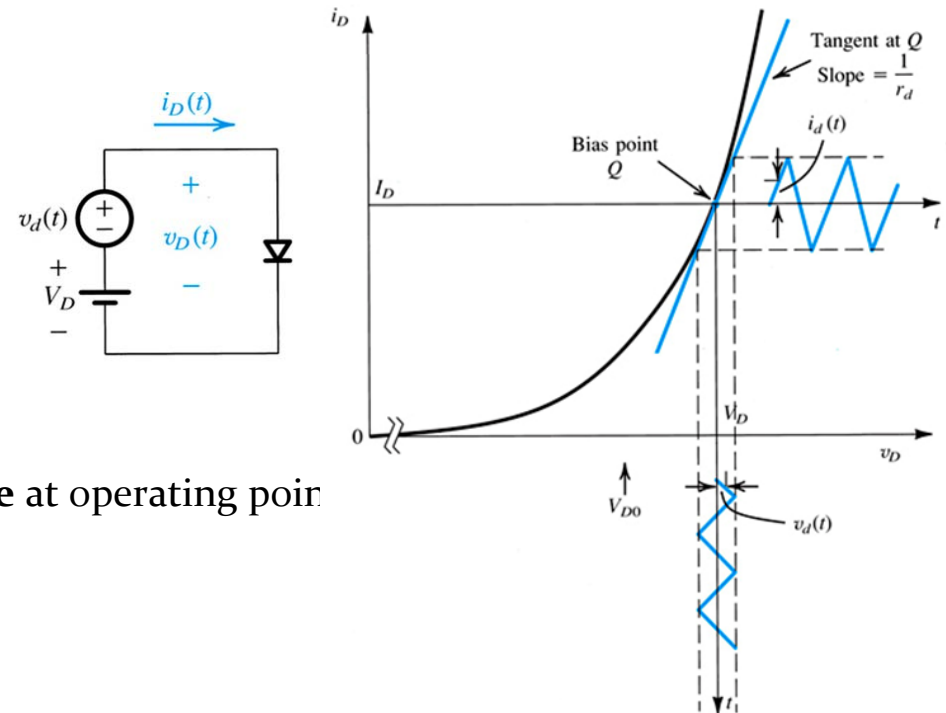
$$\rightarrow r_d = \frac{nV_T}{I_D} = 1 / \left[\frac{\partial i_D}{\partial v_D} \right]_{i_D=I_D}$$



The diode small-signal model


- Choose proper dc analysis technique or model to obtain the operation point Q
- The small-signal model is determined once Q is provided
- The small-signal model is used for circuit analysis when the diode is operating around Q

Circuit analysis techniques for total quantities (AC+DC)

- ❑ Eliminate all the time varying signals (ac voltage and current sources) for operation point analysis
- ❑ Use rapid analysis or accurate analysis to obtain dc voltage and current at operating point Q
- ❑ Determine the parameters of small-signal models from Q
- ❑ Replace the devices with small-signal models and eliminate all the dc sources
- ❑ Circuit analysis under small-signal approximation
- ❑ The complete response of the circuit is obtained by superposition of the dc and ac components

Voltage regulator by diode forward drop

- ❑ A regulator is to provide a constant dc voltage regardless changes in load and power-supply voltage
- ❑ The forward-voltage drop remains almost constant at 0.7 V within a wide current range
- ❑ Multiple diodes in series to achieve the required voltage drop
- ❑ Better regulation can be provided for higher bias current and smaller r_d

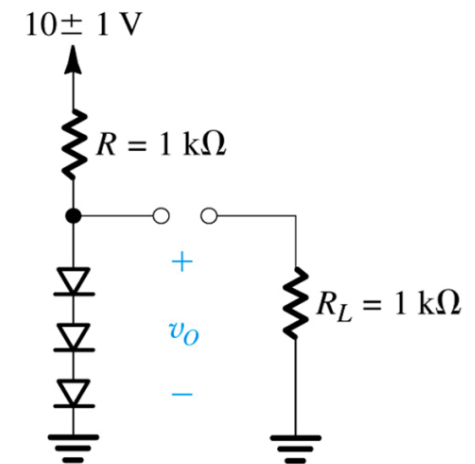

Example 3.5 (Textbook)



Example 3.6 (Textbook)

Exercise 3.14 (Textbook)

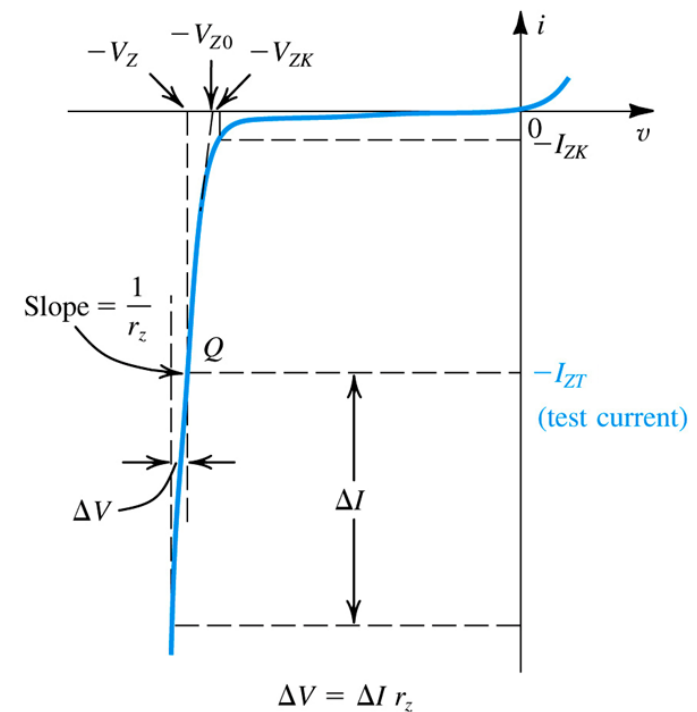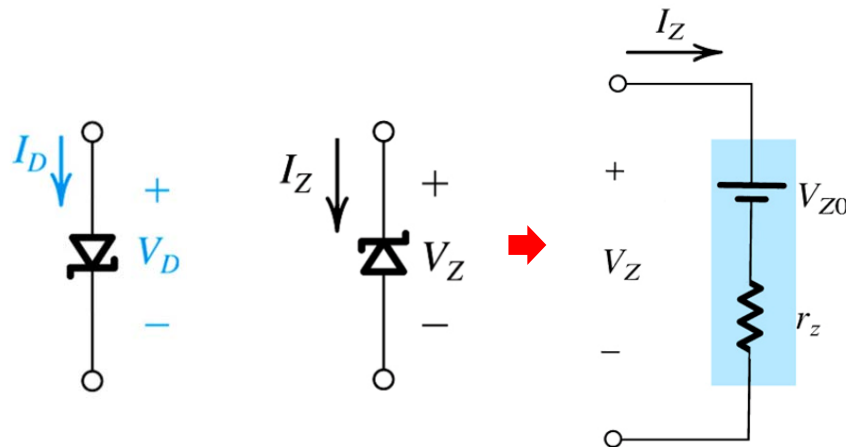3.4 Operation in the Reverse Breakdown Region – Zener Diodes

Symbol and circuit model for the Zener diode

- In breakdown region, a reverse bias (V_Z) beyond the knee voltage (V_{ZK}) leads to a large reverse current (I_Z).
- The diode in breakdown region is given by $V_Z = V_{Z0} + r_z I_Z$
 - The breakdown diode is modeled by a voltage source V_{Z0} in series with an incremental resistance r_z
 - Incremental voltage versus current: $\Delta V = r_z \Delta I$
 - The simplified model is only valid for $I_Z > I_{ZK}$ (knee current)
 - Equivalent r_z increases as I_Z decreases
- Diode types:
 - Diode: only forward and reverse regions are considered
 - Zener diode: forward, reverse and breakdown regions



Design of the Zener shunt regulator

□ Output voltage of the regulator:

$$V_o = \frac{R}{R+r_z} V_{Z0} + \frac{r_z}{R+r_z} V^+ - \frac{Rr_z}{R+r_z} I_L$$

■ **Line regulation:** $\frac{\Delta V_o}{\Delta V^+} = \frac{r_z}{R+r_z}$

■ **Load regulation:** $\frac{\Delta V_o}{\Delta I_L} = -\frac{Rr_z}{R+r_z}$


□ Line and load regulation should be minimized

□ For $r_z \ll R$, line regulation can be minimized by choosing small r_z

□ Load regulation can be minimized by choosing small r_z and large R

□ There is an upper limit on the value of R to ensure sufficiently high current I_Z (r_z increases if I_Z is too low)

□ R should be selected from $R = \frac{V_{S\min} - V_{Z0} - r_z I_{Z\min}}{I_{Z\min} + I_{L\max}}$

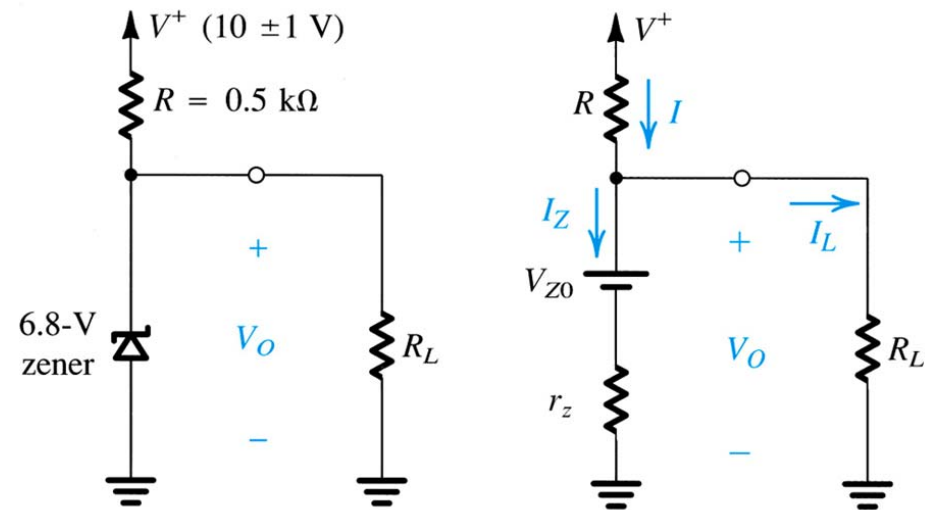

Example 3.7 (Textbook)

Exercise 3.16 (Textbook)

Exercise 3.17 (Textbook)


Exercise 3.18 (Textbook)

3.5 Rectifier Circuits

Block diagram of a dc power supply

☐ DC power supply

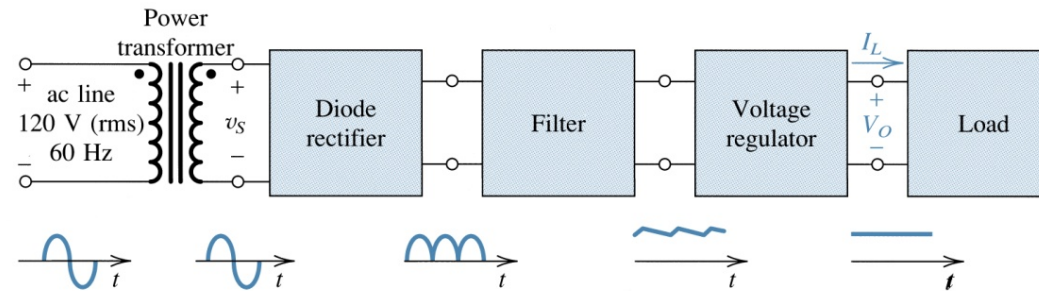- Generate a dc voltage from ac power sources
- The ac input is a low-frequency **large-signal** voltage



☐ Power transformer

- Step the line voltage down to required value and provides electric isolation

☐ Diode rectifier

- Converts the input sinusoidal to a **unipolar output**
- Can be divided to **half-wave** and **full-wave rectifiers**

☐ Filter

- Reduces the magnitude variation for the rectifier output
- Equivalent to time-average operation of the input waveform

☐ Voltage Regulator

- Further stabilizes the output to obtain a constant dc voltage
- Can be implemented by Zener diode circuits

The half-wave rectifier

□ Voltage transfer curve:

$$v_S < V_{D0} \rightarrow v_O = 0$$



$$v_S \geq V_{D0} \rightarrow v_O = v_S - V_{D0}$$

□ Rectifier diode specifications:

■ Current-handling capability: the largest current the diode is expected to conduct

■ **Peak inverse voltage (PIV)**: the largest reverse voltage the diode can stand without breakdown

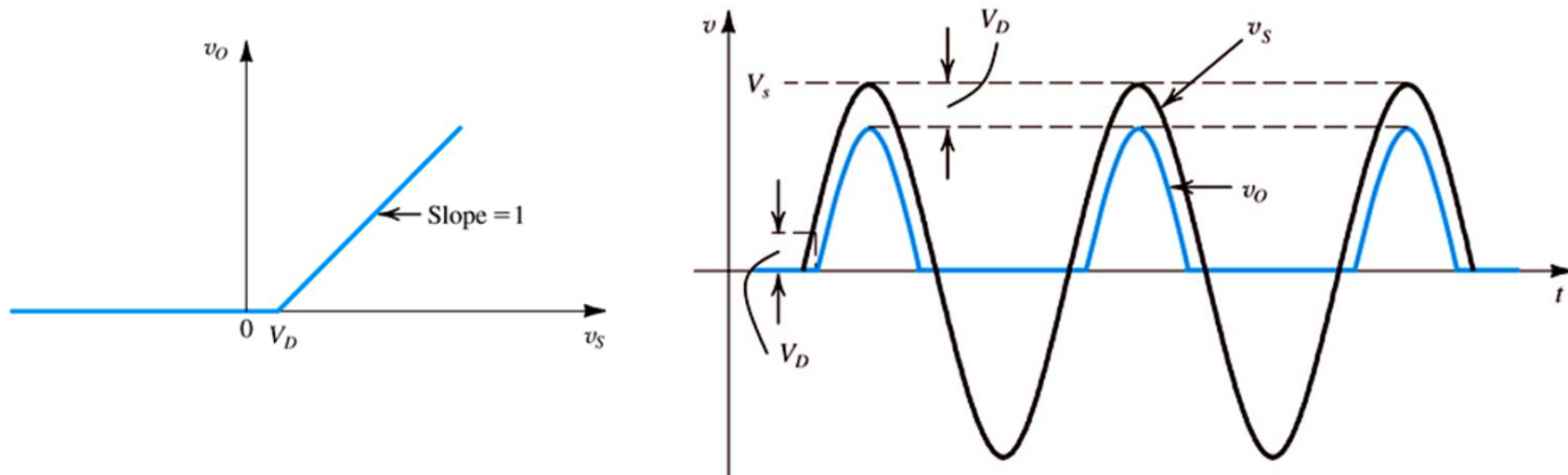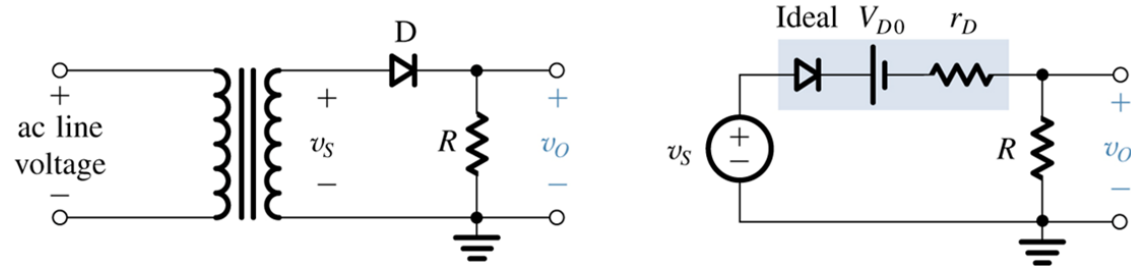□ PIV = V_s (input voltage swing) and the diode breakdown voltage is selected at least 50% higher



The full-wave rectifier (center-tapped transformer)

□ Voltage transfer curve:

$$|v_s| < V_{D0} \rightarrow v_o = 0$$






$$v_s \leq -V_{D0} \rightarrow v_o = -v_s - V_{D0}$$

□ Transformer secondary winding is center-tapped

□ Peak inverse voltage (PIV) = $2V_s - V_{D0}$

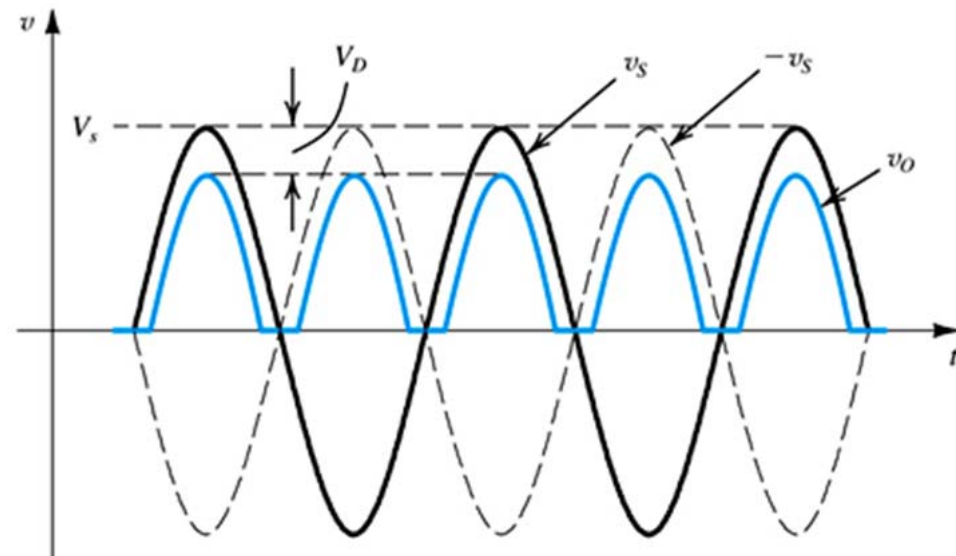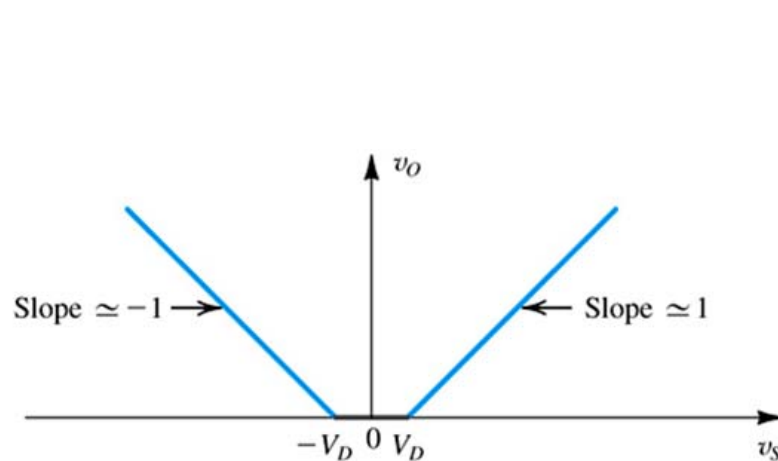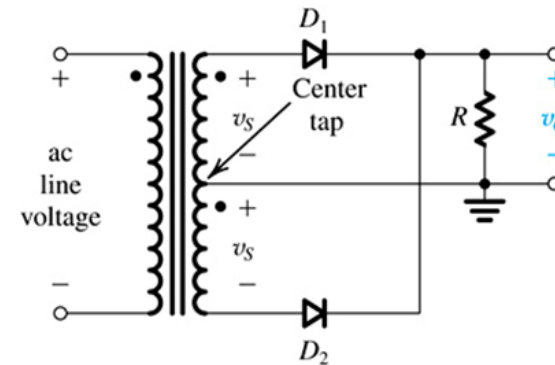□ Rectified output waveform for both positive and negative cycles



Full-wave rectifier (Bridge rectifier)

□ Voltage transfer curve:

$$|v_S| < 2V_{D0} \rightarrow v_O = 0$$

$$v_S \geq 2V_{D0} \rightarrow v_O = v_S - 2V_{D0}$$




$$v_S \leq -2V_{D0} \rightarrow v_O = -v_S - 2V_{D0}$$

□ Does not require a center-tapped transformer

□ Higher turn-on voltage ($2V_{D0}$)

□ Peak inverse voltage (PIV) = $V_S - V_{D0}$

□ Most popular rectifier circuit configuration

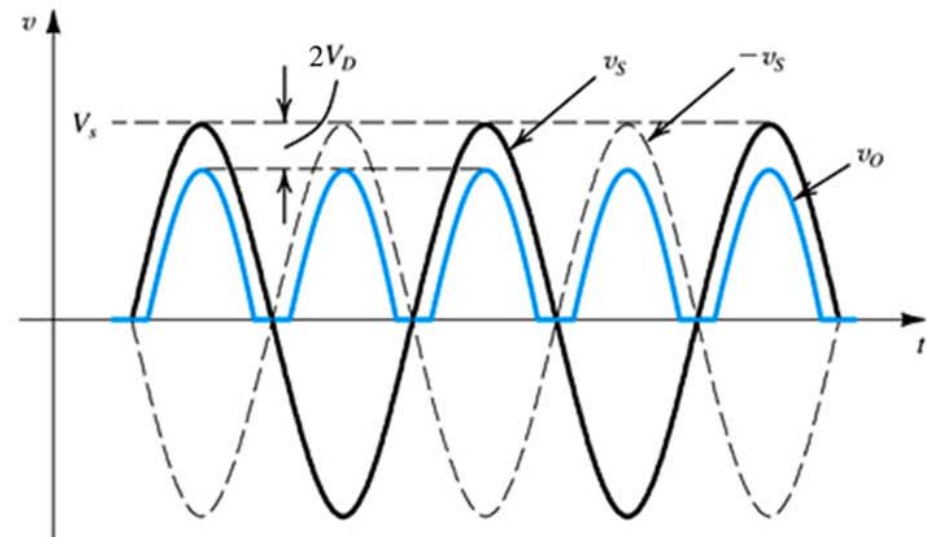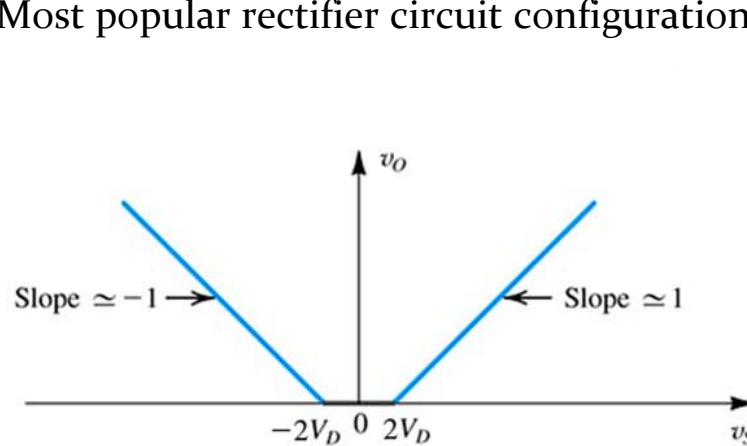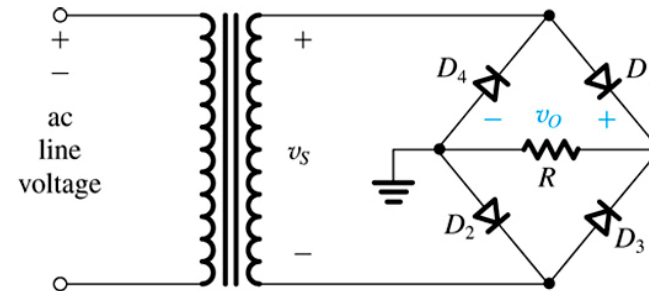



Exercise 3.19 (Textbook)

Exercise 3.20 (Textbook)



Exercise 3.21 (Textbook)

Rectifier with a filter capacitor – the peak rectifier

□ Output unloaded case:

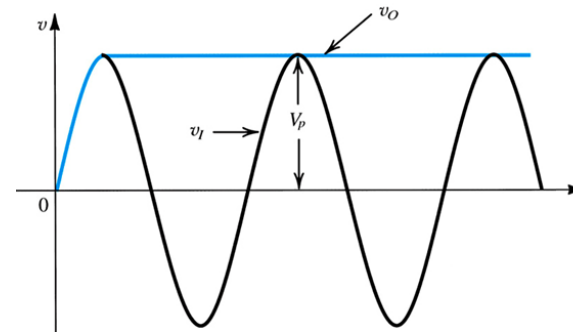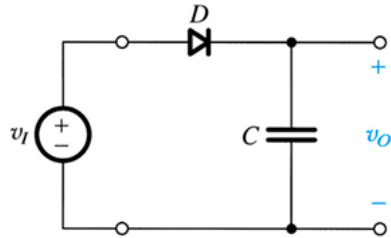


□ Output loaded case:

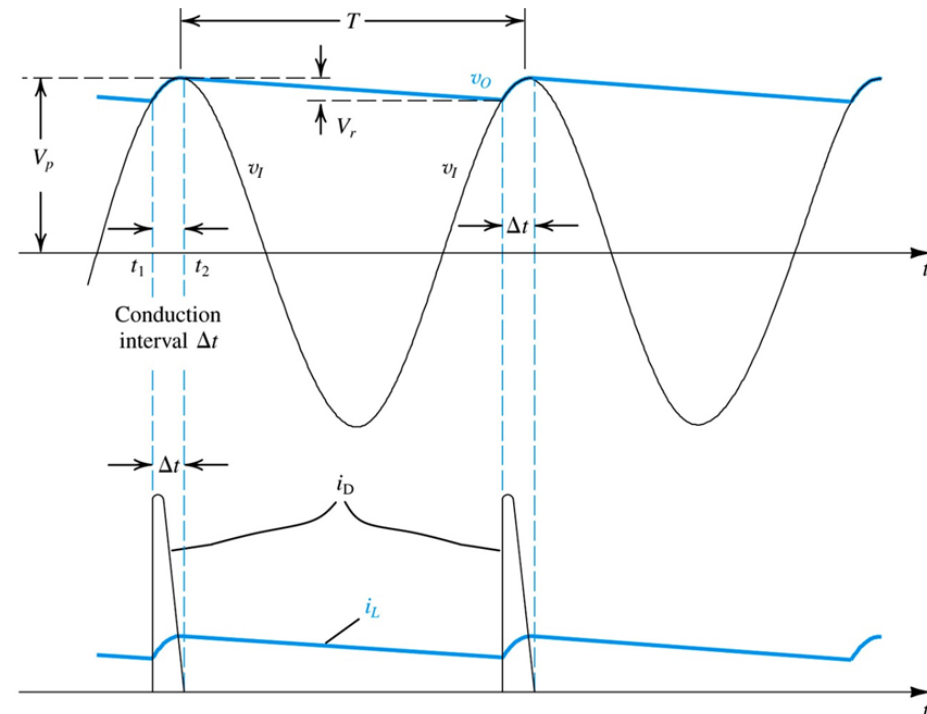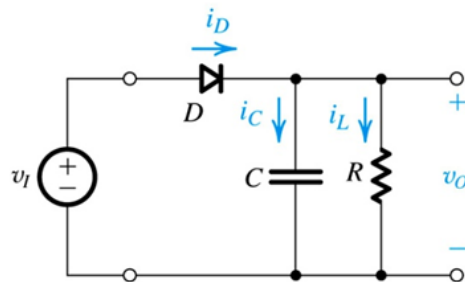

Precision half-wave rectifier – the superdiode



- ❑ Superdiode is composed of a op amp and a diode
- ❑ Superdiode works as an ideal diode with zero turn-on voltage
 - Positive input voltage:
 - ➔ Diode turns on
 - ➔ Closed-loop op amp with virtual short at input
 - ➔ Output voltage follows input voltage
 - Negative input voltage:
 - ➔ Diode turns off
 - ➔ Op amp in open loop
 - ➔ Output voltage is 0 V
- ❑ Rectifier with superdiode can demonstrate better efficiency

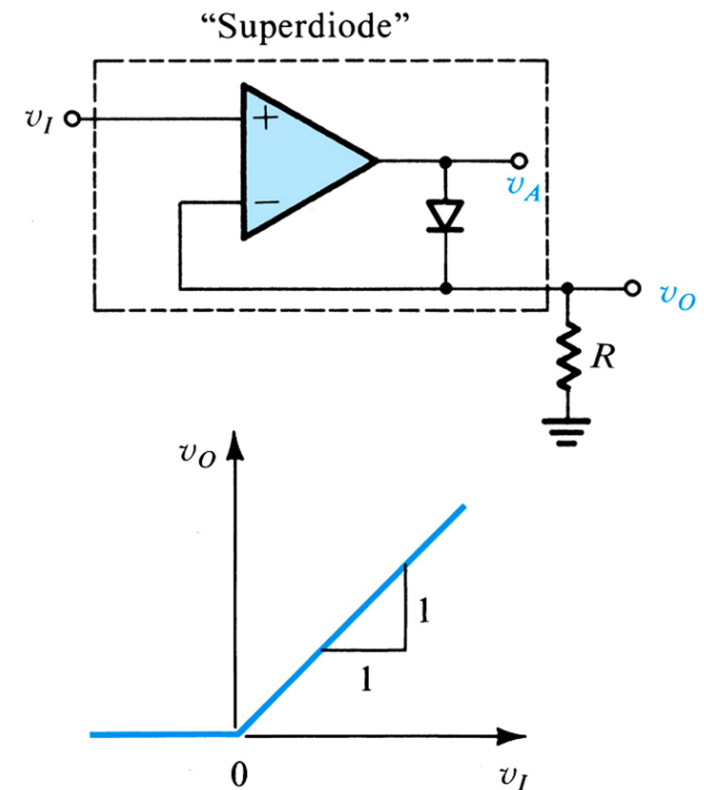

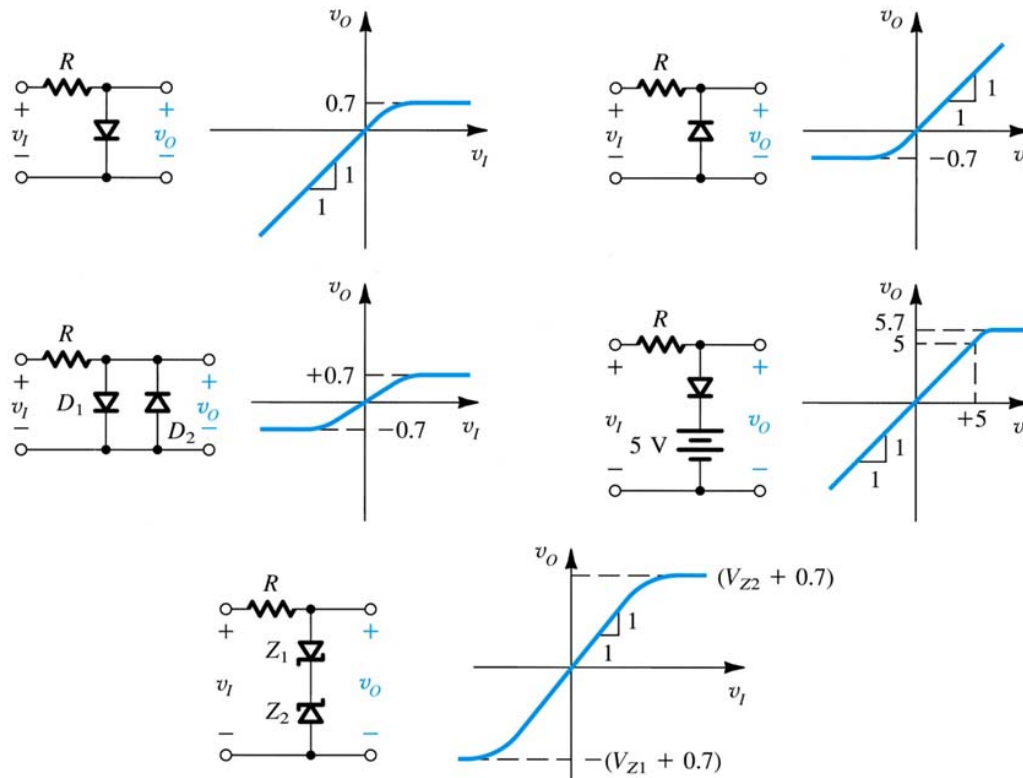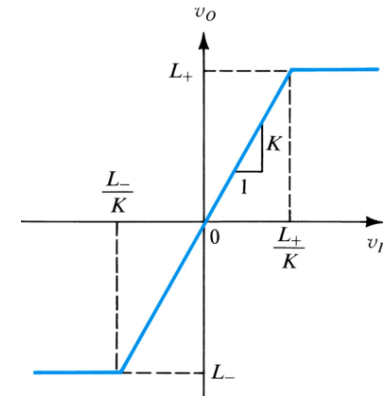3.6 Limiting and Clamping Circuits


Limiter circuits

- ❑ For input in a certain range, the limiter acts as a linear circuit.
- ❑ For input exceeds the threshold, the output voltage swing is limited.
- ❑ Classification:
 - Based on transfer characteristics: **hard limiter** and **soft limiter**
 - Based on the polarity: **single limiter** and **double limiter**
- ❑ A variety of limiting circuits by diodes:



Clamped capacitor or DC restorer

□ Output unloaded case:

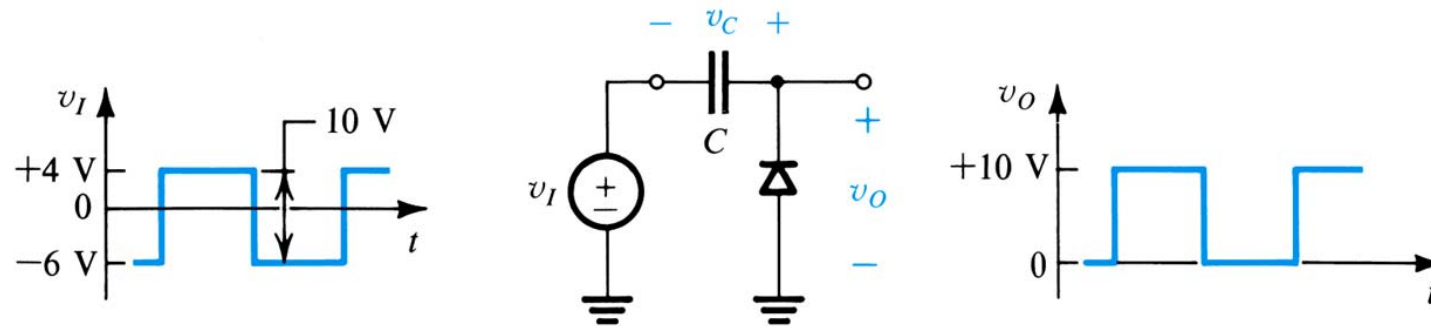

□ Output loaded case:

