



# **CHAPTER 5 MOS FIELD-EFFECT TRANSISTORS (MOSFETs)**

## **Chapter Outline**

- 5.1 Device Structure and Physical Operation
- 5.2 Current-Voltage Characteristics
- 5.3 MOSFET Circuits at DC
- 5.4 Applying the MOSFET in Amplifier Design
- 5.5 Small-Signal Operation and Models
- 5.6 Basic MOSFET Amplifier Configurations
- 5.7 Biasing in MOS Amplifier Circuits
- 5.8 Discrete-Circuit MOS Amplifiers
- 5.9 The Body Effect and Other Topics

## 5.1 Device Structure and Physical Operation

### Device structure of MOSFET

  


- ❑ “MOS”  $\equiv$  metal-oxide-semiconductor structure
- ❑ MOSFET is a four-terminal device: gate (G), source (S), drain (D) and body (B)
- ❑ The device size (channel region) is specified by channel width ( $W$ ) and channel length ( $L$ )
- ❑ Two kinds of MOSFETs:  $n$ -channel (NMOS) and  $p$ -channel (PMOS) devices
- ❑ The device structure is basically symmetric in terms of drain and source
- ❑ Source and drain terminals are specified by the operation voltage

## Operation with zero gate voltage

- ❑ The MOS structure form a parallel-plate capacitor with gate oxide layer in the middle
- ❑ Two  $pn$  junctions (S-B and D-B) are connected as back to back diodes
- ❑ The source and drain terminals are isolated by two depletion regions without conducting current
- ❑ The operating principles will be introduced by using the  $n$ -channel MOSFET as an example


 
## Creating a channel for current flow

- ❑ Positive charges accumulate in gate as a positive voltage applies to gate electrode
- ❑ Electric field forms a depletion region by pushing holes in  $p$ -type substrate away from the surface
- ❑ Electrons accumulate on the substrate surface as gate voltage exceeds a **threshold voltage**  $V_t$
- ❑ The induced  $n$  region thus forms a **channel** for current flow from drain to source
- ❑ The channel is created by inverting the substrate surface from  $p$ -type to  $n$ -type → **inversion layer**
- ❑ The field controls the amount of charge in the channel and determines the channel conductivity





## Applying a small drain voltage

- ❑ A positive  $v_{GS} > V_t$  is used to induce the channel  $\rightarrow$   $n$ -channel **enhancement-type** MOSFET
- ❑ Free electrons travel from source to drain through the induced  $n$ -channel due to a small  $v_{DS}$
- ❑ The current  $i_D$  flows from drain to source (opposite to the direction of the flow of negative charge)
- ❑ The current is proportional to the number of carriers in the induced channel
- ❑ The channel is controlled by the **effective voltage** or **overdrive voltage**:  $v_{OV} \equiv v_{GS} - V_t$
- ❑ The electron charge in the channel due to the overdrive voltage:  $|Q| = C_{ox} W L v_{OV}$
- ❑ **Gate oxide capacitance**  $C_{ox}$  is defined as capacitance per unit area
- ❑ MOSFET can be approximated as a linear resistor in this region with a resistance value inversely proportional to the excess gate voltage

  
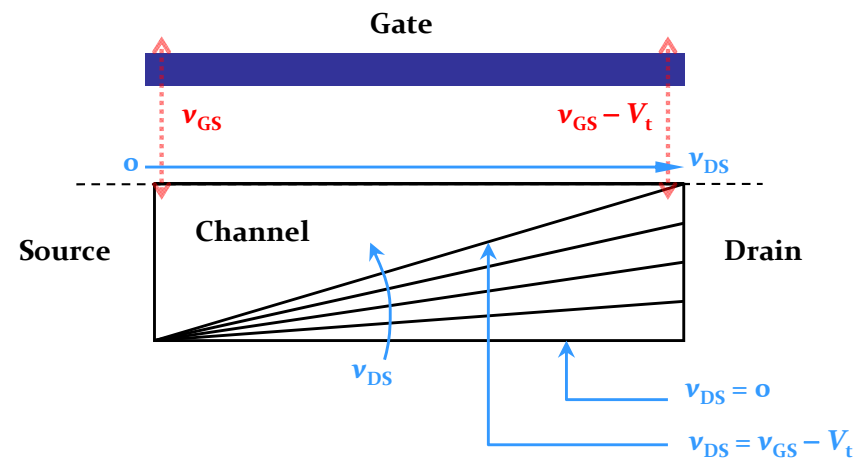 
## Operation as increasing drain voltage

- ❑ As  $v_{DS}$  increases, the voltage along the channel increases from 0 to  $v_{DS}$
- ❑ The voltage between the gate and the points along the channel decreases from  $v_{GS}$  at the source end to  $(v_{GS}-v_{DS})$  at the drain end
- ❑ Since the inversion layer depends on the voltage difference across the MOS structure, increasing  $v_{DS}$  will result in a tapered channel
- ❑ The resistance increases due to tapered channel and the  $i_D$ - $v_{DS}$  curve is no longer a straight line
- ❑ At the point  $v_{DSsat} = v_{GS} - V_t$ , the channel is **pinched off** at the drain side
- ❑ Increasing  $v_{DS}$  beyond this value has little effect on the channel shape and  $i_D$  saturates at this value
- ❑ **Triode region:**  $v_{DS} < v_{DSsat}$
- ❑ **Saturation region:**  $v_{DS} \geq v_{DSsat}$



## Derivation of the I-V relationship

- Induced charge in the channel due to MOS capacitor:

$$Q_I(x) = -C_{ox}[v_{GS} - V_t - v(x)]$$

- Equivalent resistance  $dR$  along the channel:

$$dR = \frac{dx}{qn(x)\mu_n h(x)W} = \frac{dx}{\mu_n W Q_I(x)}$$

- I-V derivations:

$$dv = i_D dR = \frac{i_D dx}{\mu_n W Q_I(x)} = \frac{i_D dx}{\mu_n C_{ox} W [v_{GS} - V_t - v(x)]}$$

$$\int_0^{v_{DS}} \mu_n C_{ox} W [v_{GS} - V_t - v(x)] dv = \int_0^L i_D dx$$

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

- Process transconductance parameter ( $\mu A/V^2$ ):  $k'_n = \mu_n C_{ox}$

- Aspect ratio:  $W/L$

- Transconductance parameter ( $\mu A/V^2$ ):  $k_n = \mu_n C_{ox} (W/L)$



- Drain current of MOSFETs:

- Triode region:  $i_D = k_n [(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2]$

- Saturation region:  $i_{Dsat} = \frac{1}{2} k_n (v_{GS} - V_t)^2$

- On-resistance (channel resistance for small  $v_{DS}$ ):

$$r_{DS} = 1/k_n (v_{GS} - V_t)$$

 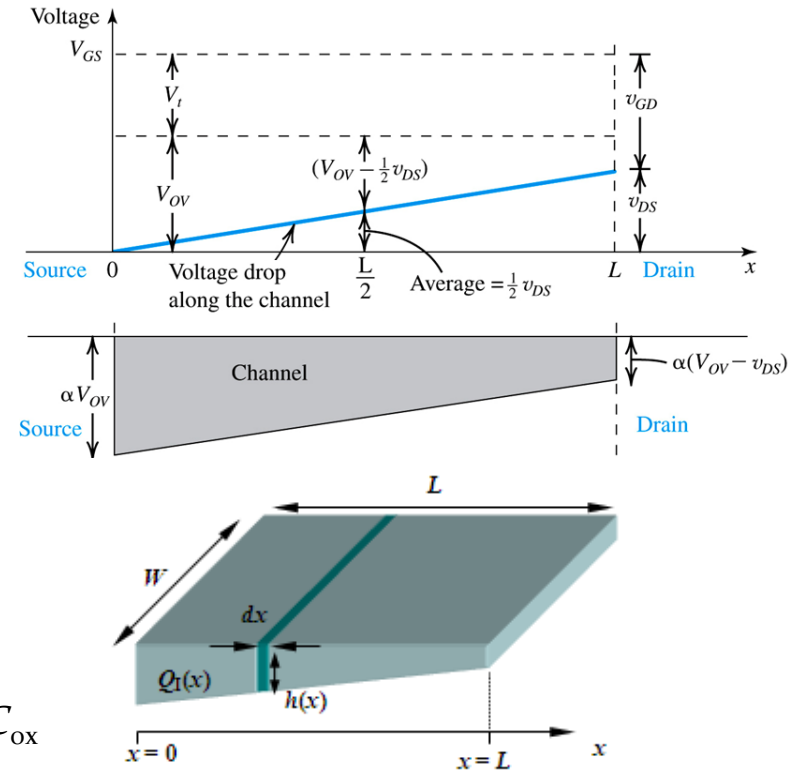

## The *p*-channel enhancement-type MOSFET


- ❑ *p*-channel enhanced-type MOSFETs are fabricated on *n*-type substrate with  $p^+$  source and  $p^+$  drain
- ❑ Normally, source is connected to high voltage and drain is connected to low voltage
- ❑ As a negative voltage applies to the gate, the resulting field pushes electrons in *n*-type substrate away from the surface, leaving behind a carrier-depletion region
- ❑ As gate voltage exceeds a negative **threshold voltage**  $V_t$ , holes accumulate on the substrate surface
- ❑ A *p*-type channel (**inversion layer**) is induced for current flow from source to drain
- ❑ Negative gate voltage is required to induce the channel → **enhancement-type** MOSFET

## Complementary MOS (CMOS)

- ❑ CMOS technology employs both PMOS and NMOS devices
- ❑ If substrate is *p*-type, PMOS transistors are formed in *n* well (*n*-type body needed)
- ❑ If substrate is *n*-type, NMOS transistors are formed in *p* well (*p*-type body needed)
- ❑ The substrate and well are connected to voltages which reverse bias the junctions for device isolation

Exercise 5.1 (Textbook)


Exercise 5.2 (Textbook)

 

## 5.2 Current-Voltage Characteristics

### Circuit symbol

□ *n*-channel enhancement-mode MOSFET

 

### The current-voltage characteristics

□ Cut-off region: ( $v_{GS} \leq V_t$ )

$$\rightarrow i_D = 0$$




□ Triode region: ( $v_{GS} > V_t$  and  $v_{DS} < v_{GS} - V_t$ )

$$\rightarrow i_D = \mu_n C_{ox} \frac{W}{L} [(v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2]$$

□ Saturation: ( $v_{GS} > V_t$  and  $v_{DS} \geq v_{GS} - V_t$ )

$$\rightarrow i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2$$

□ large-signal model (saturation)

   




## Channel length modulation

- ❑ The channel pinch-off point moves slightly away from drain as  $v_{DS} > v_{DSsat}$
- ❑ The effective channel length ( $L_{eff}$ ) reduces with  $v_{DS}$
- ❑ Electrons travel to pinch-off point will be swept to drain by electric field
- ❑ The length accounted for conductance in the channel is replaced by  $L_{eff}$ :

$$\int_0^{v_{GS}-V_t} k'_n W [v_{GS} - V_t - v(x)] dv = \int_0^{L_{eff}} i_D dx$$



$$i_D = \frac{1}{2} k'_n \frac{W}{L_{eff}} (v_{GS} - V_t)^2 = \frac{1}{2} k'_n \frac{W}{L - \Delta L} (v_{GS} - V_t)^2 \approx \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 (1 + \frac{\Delta L}{L})$$

 assuming that  $\frac{\Delta L}{L} \propto v_{DS} \rightarrow i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$


  
## Finite output resistance

$$r_o \equiv \left[ \frac{\partial i_D}{\partial v_{DS}} \right]_{v_{GS}=constant}^{-1} = \left[ \lambda \frac{k'_n W}{2 L} (v_{GS} - V_t)^2 \right]^{-1} \approx \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$$



- ❑  $V_A$  (**Early voltage**) =  $1/\lambda$  is proportional to channel length:  $V_A = V'_A L$
- ❑  $V'_A$  is process-technology dependent with a typical value from 5 ~ 50 V/ $\mu\text{m}$
- ❑ Due to the dependence of  $i_D$  on  $v_{DS}$ , MOSFET shows **finite output resistance** in saturation region

## The body effect

- ❑ The BS and BD junction should be reverse biased for the device to function properly
- ❑ Normally, the body of a  $n$ -channel MOSFET is connected to the most negative voltage
- ❑ The depletion region widens in BS and BD junctions and under the channel as  $V_{SB}$  increases
- ❑ **Body effect:**  $V_t$  increases due to the excess charge in the depletion region under the channel
- ❑ The body effect can cause considerable degradation in circuit performance
- ❑ Threshold voltage:


$$V_t = V_{t0} + \gamma [\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}]$$

$$\text{where } \gamma = \frac{\sqrt{2qN_A\epsilon_{Si}}}{C_{ox}} \text{ and } \phi_f = \frac{kT}{q} \ln\left(\frac{N_A}{n_i}\right)$$

- ❑ Current equations:

$$i_D = \mu_n C_{ox} \frac{W}{L} [(v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2]$$
 
$$i_{Dsat} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2$$



## Temperature effect

- ❑  $V_t$  decreases by  $\sim 2\text{mV}$  for every  $1^\circ\text{C}$  rise  $\rightarrow i_D$  increases with temperature
- ❑  $k'_n$  decreases with temperature  $\rightarrow i_D$  decreases with increasing temperature
- ❑ For a given bias voltage, the overall observed effect of a temperature increase is a decrease in  $i_D$

## **Breakdown and input protection**

### **❑ Weak avalanche**

- $pn$  junction between the drain and substrate suffers avalanche breakdown as  $V_{DS}$  increases
- Large drain current is observed
- Typical breakdown voltage 20 ~ 150 V

### **❑ Punch-through**

- Occurs at lower voltage (~20 V) for short channel devices
- Drain current increases rapidly as the drain depletion region extends through the channel
- Does not result in permanent damage to the device


### **❑ Gate-oxide breakdown**

- Gate-oxide breakdown occurs when gate-to-source voltage exceeds 30 V
- Permanent damage to the device

### **❑ Input Protection**

- Protection circuit is needed for the input terminals of MOS integrated circuits
- Using clamping diode for the input protection
 
## The *p*-channel enhancement-type MOSFET



- ❑ For a PMOS, the source is connected to high voltage and the drain is connected to low voltage
- ❑ To induce the *p*-channel for the MOSFET, a negative  $v_{GS}$  is required  $\rightarrow V_t$  (threshold voltage)  $< 0V$
- ❑ The body is normally connected to the most positive voltage

## The current-voltage characteristics

- ❑ Cut-off region: ( $v_{GS} \geq V_{tp}$ )

$$\rightarrow i_D = 0$$

- ❑ Triode region: ( $v_{GS} < V_{tp}$  and  $v_{DS} > v_{GS} - V_{tp}$ )

$$\rightarrow i_D = \mu_p C_{ox} \frac{W}{L} [(v_{GS} - V_{tp})v_{DS} - \frac{1}{2}v_{DS}^2]$$


- ❑ Saturation: ( $v_{GS} < V_{tp}$  and  $v_{DS} \leq v_{GS} - V_{tp}$ )

$$\rightarrow i_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (v_{GS} - V_{tp})^2$$

- ❑ Transconductance parameter  $k'_p = \mu_p C_{ox} \approx 0.4 k'_n$

- ❑ The values of  $v_{GS}$ ,  $v_{DS}$ ,  $V_t$  and  $\lambda$  for *p*-channel MOSFET operation are all negative

- ❑ Drain current  $i_D$  is still defined as a positive current

 

**Exercise 5.4 (Textbook)**

**Exercise 5.5 (Textbook)**

**Exercise 5.6 (Textbook)**


**Exercise 5.7 (Textbook)**

## 5.3 MOSFET Circuits at DC

### DC analysis for MOSFET circuits

- Assume the operation mode and solve the dc bias utilizing the corresponding current equation
- Verify the assumption with terminal voltages (cutoff, triode and saturation)
- If the solution is invalid, change the assumption of operation mode and analyze again

### DC analysis example

 


Assuming MOSFET in saturation

$$-V_{SS} = V_{GS} + I_D R_S = V_{GS} + \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 R_S$$

$$\rightarrow V_{GS} = 3V \text{ or } 1V (\text{not a valid solution})$$

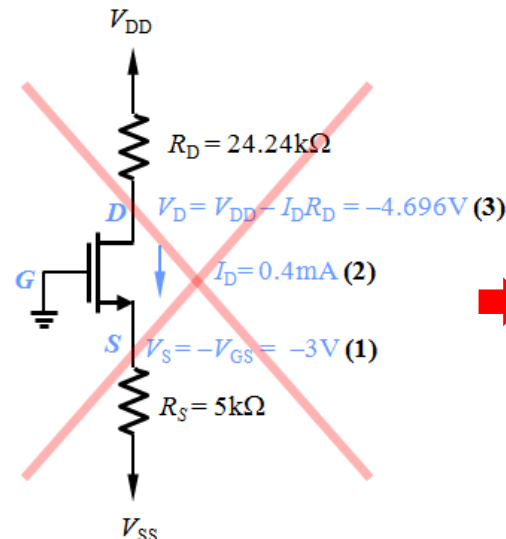
$$(V_{DS} = 4V) \geq (V_{GS} - V_t = 1V) \rightarrow \text{saturation}$$



Assuming MOSFET in saturation

$$\rightarrow V_{GS} = 3V \text{ and } V_{DS} = -1.696V$$
 
$$V_{DS} < V_{GS} - V_t \rightarrow \text{not in saturation!}$$



Assuming MOSFET in triode

$$I_D = k_n' \frac{W}{L} [(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2]$$

$$V_{GS} + I_D R_S = -V_{SS}$$

$$V_{DS} + I_D (R_D + R_S) = V_{DD} - V_{SS}$$

$$\rightarrow V_{GS} = 3.35V, V_{DS} = 0.35V \text{ and } I_D = 0.33mA$$

$$V_{DS} < V_{GS} - V_t \rightarrow \text{in triode}$$

**Exercise 5.8 (Textbook)**

**Exercise 5.9 (Textbook)**

**Exercise 5.10 (Textbook)**

**Example 5.5 (Textbook)**

**Example 5.6 (Textbook)**

**Exercise 5.12 (Textbook)**

**Example 5.7 (Textbook)**

**Example 5.8 (Textbook)**

## 5.4 Applying the MOSFET in Amplifier Design

### MOSFET voltage amplifier

□ MOSFET with a resistive load  $R_D$  can be used as a voltage amplifier

□ The voltage transfer characteristic (VTC)

■ The plot of  $v_I$  ( $v_{GS}$ ) versus  $v_O$  ( $v_{DS}$ )

■ DC analysis as  $v_{GS}$  increases from 0 to  $V_{DD}$

■ Cutoff mode: ( $0 \leq v_{GS} < V_t$ )

$$\rightarrow i_D = 0$$

$$\rightarrow v_O = v_{DS} = V_{DD}$$

■ Saturation mode: ( $v_{GS} > V_t$ )



$$\rightarrow i_D = \frac{1}{2} k_n (v_{GS} - V_t)^2$$

$$\rightarrow v_O = v_{DS} = V_{DD} - \frac{1}{2} k_n (v_{GS} - V_t)^2 R_D$$

■ Triode mode: ( $v_{GS}$  further increases)

$$\rightarrow i_D = k_n [(v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2]$$
  
$$\rightarrow v_O = v_{DS} = V_{DD} - k_n [(v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2] R_D$$





## Biasing the MOSFET to obtain linear amplification

- ❑ The slope in the VTC indicates voltage gain
- ❑ MOSFET in saturation can be used as voltage amplification
- ❑ Point Q is known as **bias point** or **dc operating point**

$$\rightarrow V_{DS} = V_{DD} - \frac{1}{2} k_n (V_{GS} - V_t)^2 R_D$$

- ❑ The signal to be amplified is superimposed on  $V_{GS}$ 
  - $\rightarrow v_{GS}(t) = V_{GS} + v_{gs}(t)$
- ❑ The time-varying part in  $v_{GS}(t)$  is the amplified signal
- ❑ The circuit can be used as a linear amplifier if:
  - A proper bias point is chosen for gain
  - The input signal is small in amplitude


## The small-signal voltage gain

- ❑ The amplifier gain is the slope at Q:

$$A_v \equiv \left. \frac{dv_{DS}}{dv_{GS}} \right|_{v_{GS}=V_{GS}} = -k_n (V_{GS} - V_t) R_D = -k_n V_{OV} R_D$$

- ❑ Maximum voltage gain of the amplifier

$$|A_v| = \left| -\frac{I_D R_D}{V_{OV}/2} \right| < \frac{V_{DD}}{V_{OV}/2} = |A_{v\max}|$$

 

## Determining the VTC by graphical analysis



- ❑ Provides more insight into the circuit operation
- ❑ **Load line:** the straight line represents in effect the load

$$\rightarrow i_D = (V_{DD} - v_{DS})/R_D$$

- ❑ The operating point is the intersection point
  
## Locating the bias point Q

- ❑ The bias point (intersection) is determined by properly choosing the load line
- ❑ The output voltage is bounded by  $V_{DD}$  (upper bound) and  $V_{OV}$  (lower bound)
- ❑ The load line determines the voltage gain
- ❑ The bias point determines the maximum upper/lower voltage swing of the amplifier



## 5.5 Small-Signal Operation and Models

### The DC bias point

□ MOSFET in saturation

■ Drain current:  $I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2 = \frac{1}{2} k_n V_{OV}^2$

■ Drain voltage:  $V_{DS} = V_{DD} - I_D R_D > V_{OV}$

□ The small-signal circuit parameters are determined by the bias point

### The small-signal operation

□ The small-signal drain current:

$$v_{GS} = V_{GS} + v_{gs}$$

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} + v_{gs} - V_t)^2 = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 + k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n' \frac{W}{L} v_{gs}^2$$

$$\approx \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 + k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs} = I_D + i_d$$



$$\rightarrow i_d = k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs}$$

□ The small-signal voltage gain:

$$v_D = V_{DD} - i_D R_D = V_{DD} - (I_D + i_d) R_D = V_D - i_d R_D = V_D + v_d$$

$$\rightarrow v_d = -i_d R_D = -k_n' \frac{W}{L} V_{OV} R_D v_{gs}$$
  
$$\rightarrow A_v \equiv \frac{v_d}{v_{gs}} = -k_n' \frac{W}{L} V_{OV} R_D$$



## The small-signal parameters

□ Transconductance ( $g_m$ ): describes how  $i_d$  change with  $v_{gs}$

$$g_m \equiv \frac{i_d}{v_{gs}} = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} = k'_n \frac{W}{L} (V_{GS} - V_t) = \sqrt{2k'_n \frac{W}{L} I_D}$$

□ Output resistance ( $r_o$ ): describes how  $i_d$  change with  $v_{ds}$

$$r_o \equiv \left[ \frac{\partial i_D}{\partial v_{DS}} \right]^{-1}_{v_{GS}=\text{constant}} \approx \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$$

■ Drain current varies with  $v_{DS}$  due to channel length modulation

■ Finite  $r_o$  to model the linear dependence of  $i_D$  on  $v_{DS}$

■ The effect can be neglected if  $r_o$  is sufficiently large

□ Body transconductance ( $g_{mb}$ ): describes how  $i_d$  changes with  $v_{bs}$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2$$

$$\rightarrow g_{mb} \equiv \left. \frac{\partial i_D}{\partial v_{BS}} \right|_{\substack{v_{GS}=\text{constant} \\ v_{DS}=\text{constant}}} = \frac{\partial i_D}{\partial V_t} \frac{\partial V_t}{\partial v_{BS}} = -k'_n \frac{W}{L} (v_{GS} - V_t) \frac{\partial V_t}{\partial v_{BS}} = g_m \frac{\partial V_t}{\partial v_{SB}}$$



$$V_t = V_{t0} + \gamma [\sqrt{2\phi_F + v_{SB}} - \sqrt{2\phi_F}] \text{ where } \gamma = \sqrt{2qN_A \epsilon_{Si}} / C_{ox}$$

$$\rightarrow \frac{\partial V_t}{\partial v_{SB}} \equiv \chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}}$$

$$g_{mb} = g_m \chi$$


■ The body effect of the MOSFET is modeled by  $g_{mb}$

  ■ Can be neglected if body and source are connected together




## The small-signal equivalent circuit models

### □ Hybrid- $\pi$ model

 

### □ T-model

 

### Small-Signal Parameters

#### NMOS transistors

##### ■ Transconductance:


$$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$$

##### ■ Output resistance:

$$r_o = V_A / I_D = 1 / \lambda I_D$$

## 5.6 Basic MOSFET Amplifier Configuration

### Three basic configurations

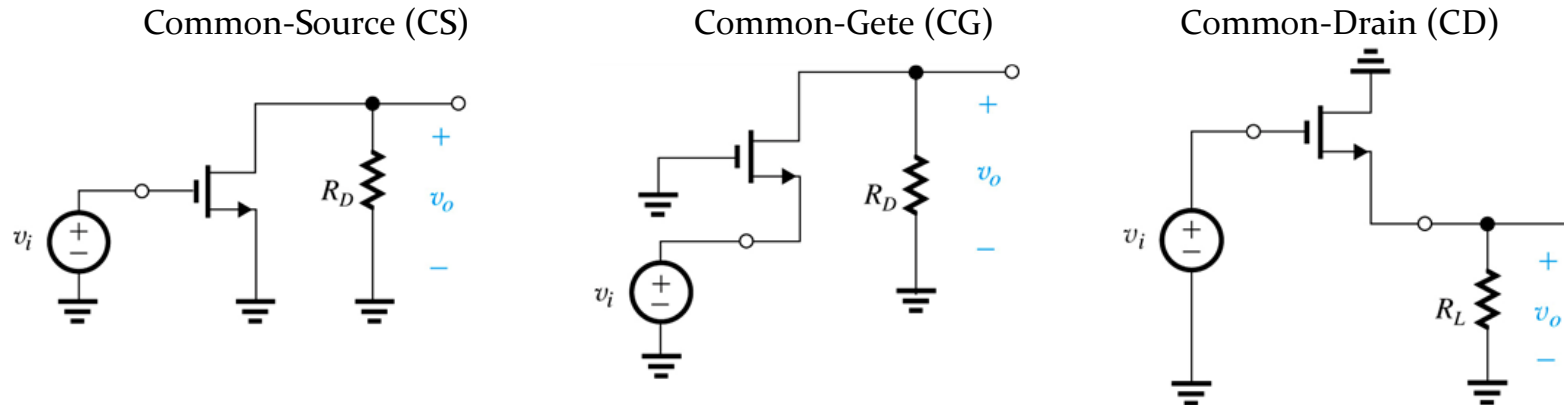


### Characterizing amplifiers

- ❑ The MOSFET circuits can be characterized by a voltage amplifier model (unilateral model)
- ❑ The electrical properties of the amplifier is represented by  $R_{in}$ ,  $R_o$  and  $A_{vo}$
- ❑ The analysis is based on the small-signal or linear equivalent circuit (dc components not included)

❑ Voltage gain:  $A_v \equiv \frac{v_o}{v_i} = \frac{R_L}{R_L + R_o} A_{vo}$

 ❑ Overall voltage gain:  $G_v \equiv \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} A_v = \frac{R_{in}}{R_{in} + R_{sig}} \frac{R_L}{R_L + R_o} A_{vo}$



## The common-source (CS) amplifier

### □ Characteristic parameters of the CS amplifier


- Input resistance:  $R_{in} = \infty$
- Output resistance:  $R_o = R_D \parallel r_o \approx R_D$
- Open-circuit voltage gain:  $A_{vo} = -g_m(R_D \parallel r_o) \approx -g_m R_D$
- Voltage gain:  $A_v = -g_m(R_D \parallel R_L \parallel r_o) \approx -g_m(R_D \parallel R_L)$

### □ CS amplifier can provide high voltage gain

### □ Input and output are out of phase due to negative gain

### □ Output resistance is moderate to high
 
### □ Small $R_D$ reduces $R_o$ at the cost of voltage gain



## The common-source (CS) with a source resistance

□ Characteristic parameters (by neglecting  $r_o$ )

■ Input resistance:

$$R_{in} = \infty$$

■ Output resistance:

$$R_o = R_D$$

■ Open-circuit voltage gain:

$$A_{vo} = -\frac{g_m R_D}{1 + g_m R_s}$$

■ Voltage gain:

$$A_v = -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$$



■ Overall voltage gain:

$$G_v = -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$$

□ Source degeneration resistance  $R_s$  is adopted

□ Gain is reduced by the factor  $(1 + g_m R_s)$

  □ Considered a negative feedback of the amplifier





## The common-gate (CG) amplifier

❑ Characteristic parameters of the CG amplifier (by neglecting  $r_o$ )

■ Input resistance:  $R_{in} = 1/g_m$

■ Output resistance:  $R_o = R_D$

■ Open-circuit voltage gain:  $A_{vo} = g_m R_D$

■ Voltage gain:  $A_v = g_m (R_D \parallel R_L)$

■ Overall voltage gain:  $G_v = \frac{1}{1 + g_m R_{sig}} g_m (R_D \parallel R_L)$

❑ CG amplifier can provide high voltage gain

❑ Input and output are in-phase due to positive gain



❑ Input resistance is very low

❑ A single CG stage is not suitable for voltage amplification

❑ Output resistance is moderate to high

❑ Small  $R_D$  reduces  $R_o$  at the cost of voltage gain

  ❑ The amplifier is no longer unilateral if  $r_o$  is included



## The common-collector (CD) amplifier

❑ Characteristic parameters of the CD amplifier (by neglecting  $r_o$ )

■ Input resistance:  $R_{in} = \infty$

■ Output resistance:  $R_o = 1/g_m$

■ Voltage gain:  $A_v = R_L / (R_L + 1/g_m) = g_m R_L / (g_m R_L + 1) \approx 1$

■ Overall voltage gain:  $G_v = (R_L) / (R_L + 1/g_m) = g_m R_L / (g_m R_L + 1) \approx 1$



❑ CD amplifier is also called **source follower**.

❑ Input resistance is very high

❑ Output resistance is very low

❑ The voltage gain is less than but can be close to 1

  ❑ CD amplifier can be used as voltage buffer



## 5.7 Biasing in MOS Amplifier Circuits

### DC bias for MOSFET amplifier


- ❑ The amplifiers are operating at a proper dc bias point
- ❑ Linear signal amplification is provided based on small-signal circuit operation
- ❑ The DC bias circuit is to ensure the MOSFET in **saturation** with a proper collector current  $I_D$

### Biasing by fixing gate-to-source voltage

- ❑ Fix the dc voltage  $V_{GS}$  to specify the saturation current of the MOSFET:  $I_D = \frac{1}{2}k_n(V_{GS} - V_t)^2 = \frac{1}{2}k_n(V_G - V_t)^2$
- ❑ Bias current deviates from the desirable value due to variations in the device parameters  $V_t$  and  $\mu_n$

 
### Biasing by fixing gate voltage and connecting a source resistance

- ❑ The bias condition is specified by:  $V_G = V_{GS} + \frac{1}{2}k_n(V_{GS} - V_t)^2 R_S$  and  $I_D = \frac{1}{2}k_n(V_{GS} - V_t)^2$
- ❑ Drain current has better tolerance to variations in the device parameters


 
## Biasing using a drain-to-gate feedback resistor

- ❑ A single power supply is needed
- ❑  $R_G$  ensures the MOSFET in saturation ( $V_{GS} = V_{DS}$ )
- ❑ MOSFET operating point:  $\frac{V_{DD} - V_{GS}}{R_D} = \frac{1}{2} k_n (V_{GS} - V_t)^2$
- ❑ The value of the feedback resistor  $R_G$  affects the small-signal gain



## Biasing using a constant-current source

- ❑ The MOSFET can be biased with a constant current source  $I$
- ❑ The resistor  $R_D$  is chosen to operate the MOSFET in active mode
- ❑ The current source is typically a current mirror
- ❑ Current mirror circuit:


■ MOSFETs  $Q_1$  and  $Q_2$  are in saturation

■ The reference current  $I_{REF} = I = I_D$

$$\frac{V_{DD} - V_{GS}}{R} = \frac{1}{2} k_n (V_{GS} - V_t)^2$$

$$I_{REF} = \frac{1}{2} k_n (V_{GS} - V_t)^2$$

■ When applying to the amplifier circuit, the voltage  $V_{D2}$  has to be high enough to ensure  $Q_2$  in saturation

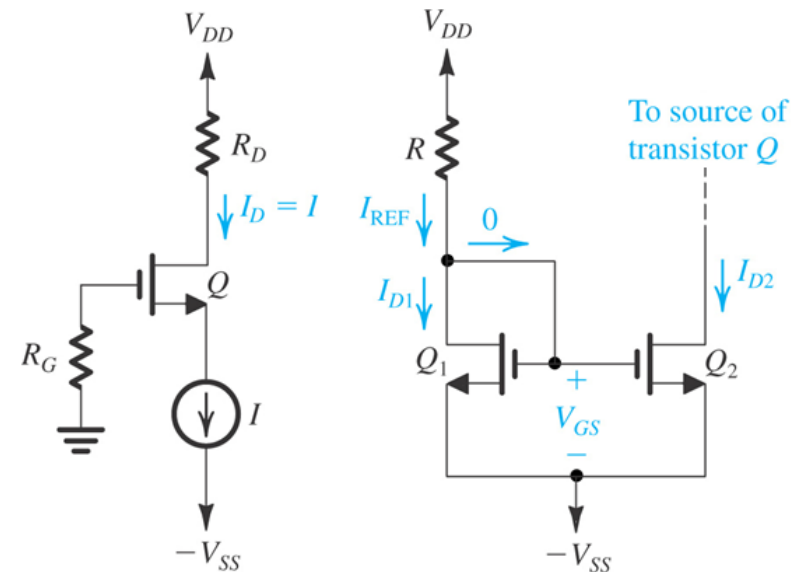

**Example 6.11 (Textbook)**

**Exercise 6.31 (Textbook)**

**Exercise 6.32 (Textbook)**

**Exercise 6.33 (Textbook)**

## 5.8 Discrete-Circuit MOS Amplifiers


### Circuit analysis:

#### □ DC analysis:



- Remove all ac sources (short for voltage source and open for current source)
- All capacitors are considered open-circuit
- DC analysis of MOSFET circuits for all nodal voltages and branch currents
- Find the dc current  $I_D$  and make sure the MOSFET is in saturation
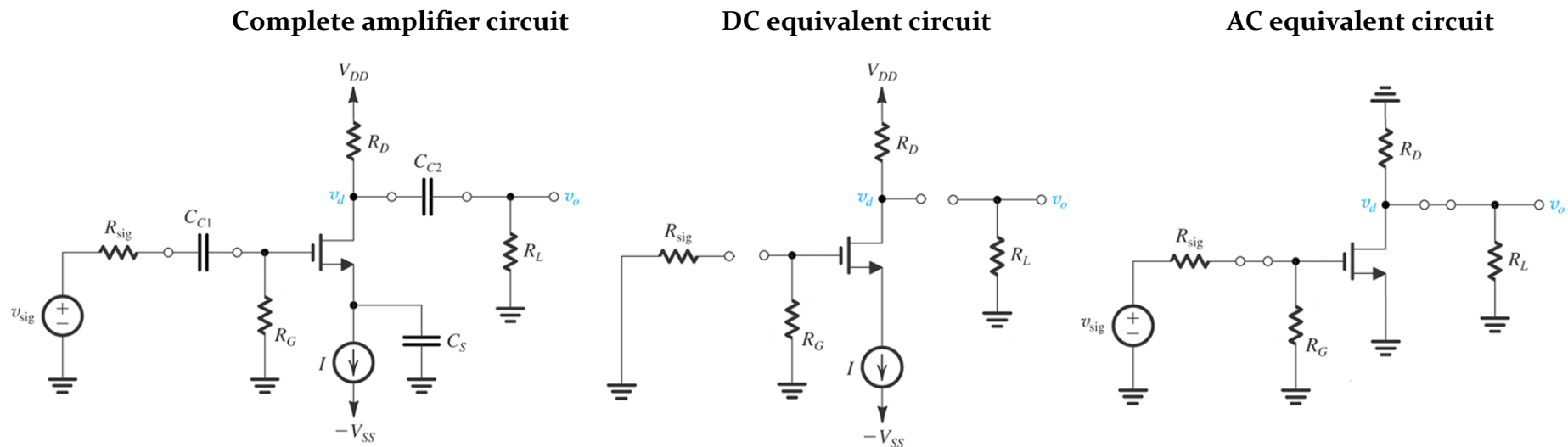
#### □ AC analysis:



- Remove all dc sources (short for voltage source and open for current source)
- All **large capacitors** are considered short-circuit
- Replace the MOSFET with its small-signal model for ac analysis
- The circuit parameters in the small-signal model are obtained based on the value of  $I_D$





## The common-source (CS) amplifier

  

 
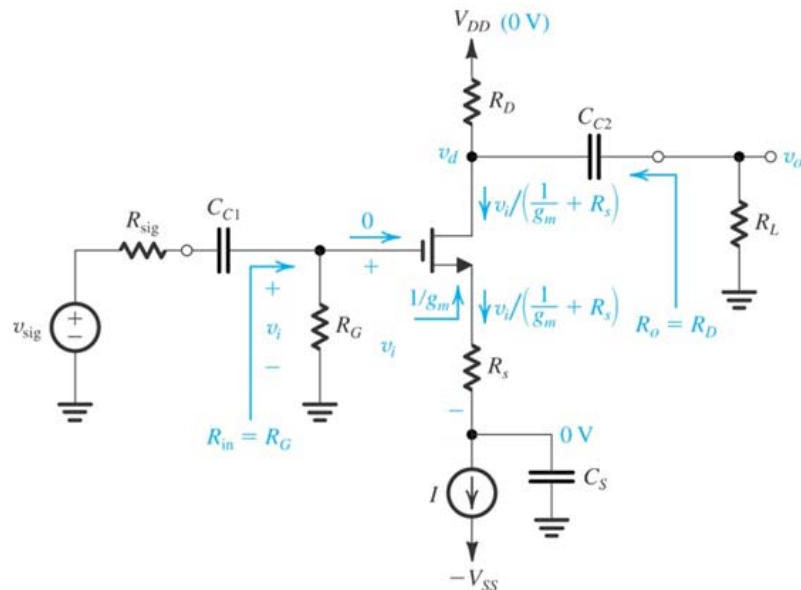
## The common-source amplifier with a source resistance



## The common-gate (CG) amplifier

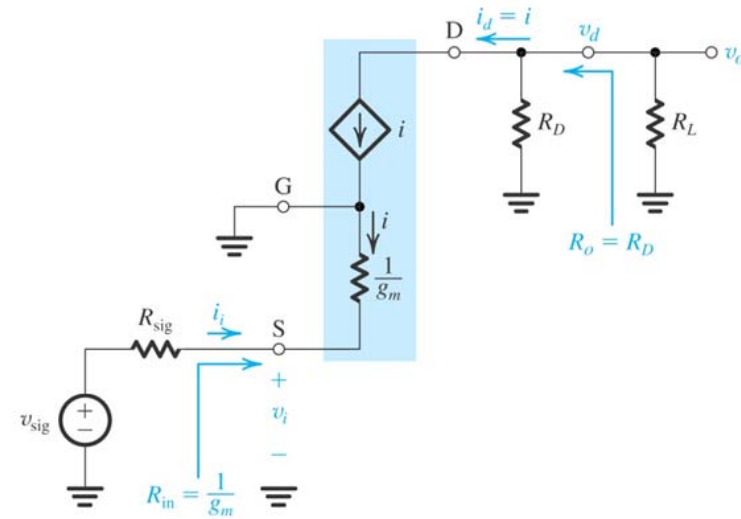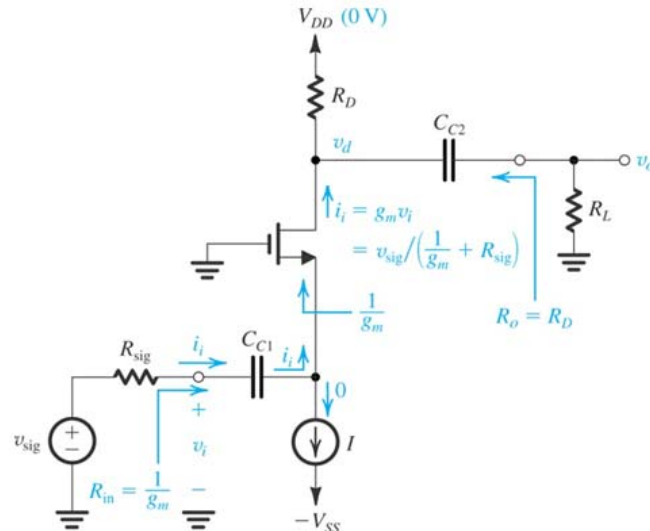


## The common-drain (CD) amplifier

  



## The amplifier frequency response

- ❑ The gain falls off at low frequency band due to the effects of the coupling and by-pass capacitors
- ❑ The gain falls off at high frequency band due to the internal capacitive effects in the MOSFETs
- ❑ Midband:
  - All coupling and by-pass capacitors (large capacitance) are considered short-circuit
  - All internal capacitive effects (small capacitance) are considered open-circuit
  - Midband gain is nearly constant and is evaluated by small-signal analysis
  - The bandwidth is defined as  $BW = f_H - f_L$
  - A figure-of-merit for the amplifier is **its gain-bandwidth product** defined as  $GB = |A_M|BW$

 

**Exercise 6.37 (Textbook)**

**Exercise 6.38 (Textbook)**

**Exercise 6.40 (Textbook)**

**Exercise 6.41 (Textbook)**

**Exercise 6.42 (Textbook)**

**Exercise 6.43 (Textbook)**

**Exercise 6.44 (Textbook)**